



# Lab 5: Character LCD Control


Chun-Jen Tsai and Lan-Da Van  
Department of Computer Science  
National Yang Ming Chiao Tung University  
Taiwan, R.O.C.  
*Fall, 2024*


 
# Lab 5: Character LCD Control

Lab 5

- ◆ In this lab, you will implement a slot machine by switches and display the results on the standard 1602 character LCD.
- ◆ The lab file submission deadline is on 10/14 by 6:00pm.





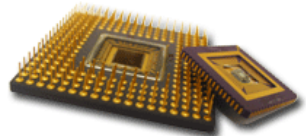
# 1602 Character LCD Display

Lab 5

- ◆ The Arty board has only simple I/O devices such as the LEDs, switches, buttons, and UART.
- ◆ We have designed an expansion board, Arty\_IO, that adds three more peripherals to Arty:
  - a 1602 character LCD device (supports only 4-bit mode)
  - a SD card socket (supports only the SPIF mode)
  - a 12-bit color VGA interface





# Memory Map of the LCD

Lab 5


- ◆ The LCD device can be treated as a 32-byte memory.
  - Each memory cell corresponds to a character on the display.
  - Writing an ASCII code to a cell will display the character on the corresponding location on the LCD:



Note: the LCD device is slow, you should not update the screen faster than 2 Hz.

- ◆ Display data memory (DD RAM) addresses:

1	00	01	02	03	04	05	06	07	08	09	0A	0B	0C	0D	0E	0F
2	40	41	42	43	44	45	46	47	48	49	4A	4B	4C	4D	4E	4F
	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15	16

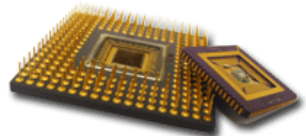




# Character LCD Interface (1/2)

Lab 5

- ◆ The LCD interface has 8 data wires (DB0 ~ DB7) and 3 control wires (LCD\_E, LCD\_RS, LCD\_RW):
  - LCD\_E enables/disables the inputs to the LCD module.
  - The rest of the wires are defined depending on the functions:

Function	LCD_RS	LCD_RW	Upper Nibble				Lower Nibble			
			DB7	DB6	DB5	DB4	DB3	DB2	DB1	DB0
Clear Display	0	0	0	0	0	0	0	0	0	1
Return Cursor Home	0	0	0	0	0	0	0	0	1	-
Entry Mode Set	0	0	0	0	0	0	0	1	I/D	S
Display On/Off	0	0	0	0	0	0	1	D	C	B
Cursor and Display Shift	0	0	0	0	0	1	S/C	R/L	-	-
Function Set	0	0	0	0	1	0	1	0	-	-
Set CG RAM Address	0	0	0	1	A5	A4	A3	A2	A1	A0
Set DD RAM Address	0	0	1	A6	A5	A4	A3	A2	A1	A0
Read Busy Flag and Address	0	1	BF	A6	A5	A4	A3	A2	A1	A0
Write Data to CG RAM or DD RAM	1	0	D7	D6	D5	D4	D3	D2	D1	D0
Read Data from CG RAM or DD RAM	1	1	D7	D6	D5	D4	D3	D2	D1	D0

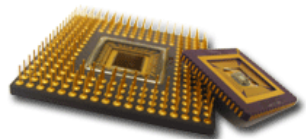



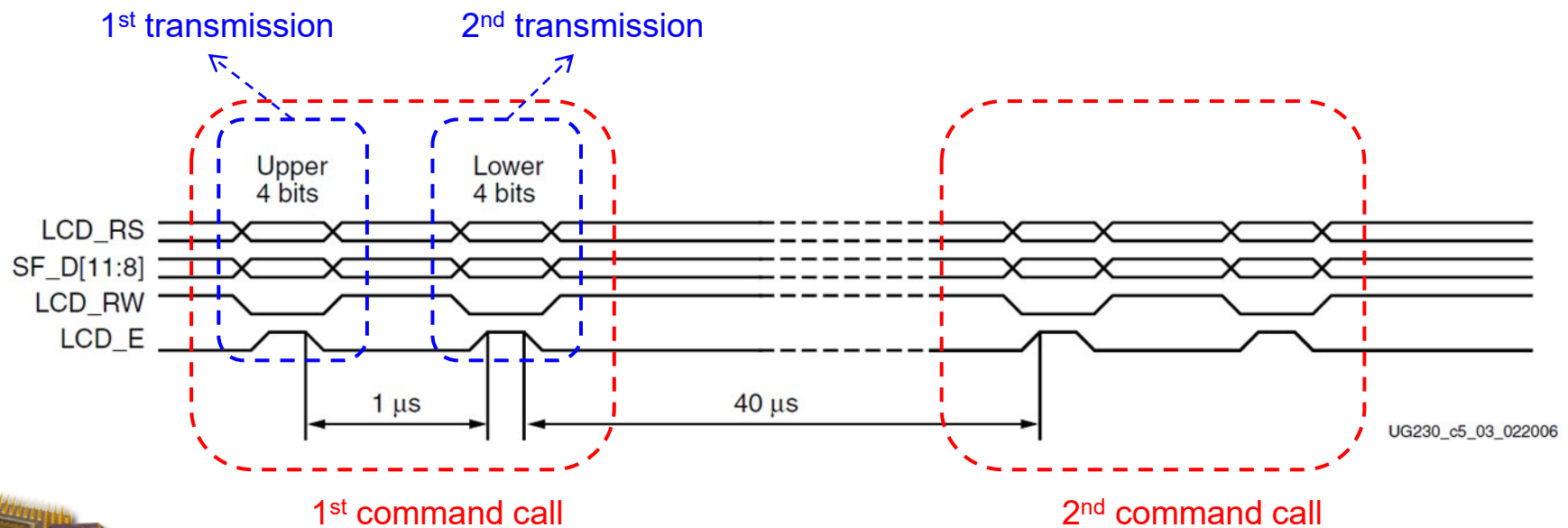
# Character LCD Interface (2/2)

Lab 5

- ◆ However, the Arty\_IO board uses the 4-bit operating mode of the LCD device, that is, only DB4~DB7 are connected to the FPGA.
  - Execution of a function will need two transmissions, using only LCD\_E, LCD\_RS, LCD\_RW, and DB4~DB7:






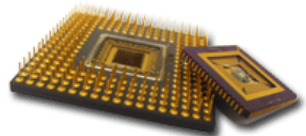 
# Timing Diagrams for Transmission

Lab 5

- ◆ The timing diagram for one transmission in four-bit mode is as follows:
  - Note that execution of a function requires two transmissions.





# Sample Circuit of Lab 5


Lab 5

- ◆ Two Verilog program files will be provided to you:
  - LCD\_Module.v – An LCD controller module (You do not need to modify this file)
  - Lab5.v – a sample top-level module that prints a “Hello, World!” message using the LCD controller module

```
module LCD_module(  
    input clk,  
    input reset,  
    input [127:0] row_A,  
    input [127:0] row_B,  
    output reg LCD_E,  
    output reg LCD_RS,    //register select  
    output reg LCD_RW,    //read / write  
    output reg [3:0] LCD_D //data  
);
```

top-row of text

bottom-row of text

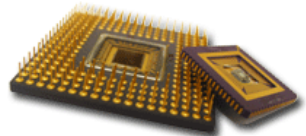





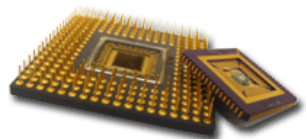
# Slot Machine

Lab 5

- ◆ In this lab, you will implement a slot machine using switches and LCD display.
- ◆ Since a casino needs to earn money, we should implement the certain rule.
- ◆ [Important] It is not wise to gambling!




## Lab 5

- 2

00	01	02	03	04	05	06	07	08	09	0A	0B	0C	0D	0E	0F
40	41	42	43	44	45	46	47	48	49	4A	4B	4C	4D	4E	4F

col1 col2 col3

 



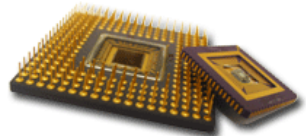
# What to Do in Lab5

Lab 5

- ◆ If all switches are pull down(low signal level), your LCD should **immediately** show some result:
  - If all the numbers of three columns are the same, your LCD should output “Jackpots!” in first row.
  - If two of the numbers of three columns are the same, your LCD should output “Free Game!” in first row.
  - If none of numbers of three columns are the same, your LCD should output “Loser!” in first row.
  - You should also show “Game over” in **second row in each case.**
- ◆ Your circuit should come back to initial status and **well-prepared for next player** when the reset button is pressed.





# What to Do in Lab5

Lab 5

- ◆ Each column of LCD should display the following number sequence:
  - First column:  $\{1,2,3,4,5,6,7,8,9,1,2,3...\}$  (scrolls up each second)
  - Second column:  $\{9,8,7,6,5,4,3,2,1,9,8,7...\}$   
(scrolls up **each two second**)
  - Third column: you can design your own number sequence! But each sequence should contains all 9 numbers  
(scrolls up each second)
- ◆ The first row in LCD should show the **future number**, while the second row in LCD should show **current number**.
- ◆ Example: assume third column is same as first column:

**Initial state**

2		8		2
1		9		1

3		8		3
2		9		2


4		7		4
3		8		3


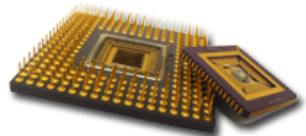
# (Advanced) What to Do in Lab5

Lab 5

- ◆ You can earn **extra 20%** on this lab by correctly implementing the advanced circuit.
- ◆ For the advanced part, we'll add a circuit to prevent misuse or cheating.





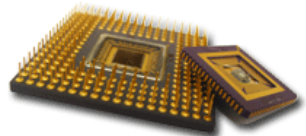
# (Advanced) What to Do in Lab5

Lab 5

- ◆ If SW1~3 are pulled down before SW0, stop the game.
- ◆ During gameplay, if any switch is pulled down and then up again, stop the game.
- ◆ Show "ERROR" on the first row and "game stopped" on the second row when these conditions occur.





# What to Do in Lab5

Lab 5

- ◆ You can assume when the circuit is first activate or reset, all switches are pulled up (high signal level).
- ◆ Your LCD should remain clear when there is no character need to be printed.
- ◆ TA will provide an demo example video on E3.
- ◆ TA would ask some questions during demo.
  - Please zip and upload the whole project including .bit file on E3 before deadline.

