



# Lab 4: Push Button and LED Control

Chun-Jen Tsai and Lan-Da Van  
Department of Computer Science  
National Yang Ming Chiao Tung University  
Taiwan, R.O.C.  
*Fall, 2024*



# Lab 4: Push Buttons and LED Control

Lab 4

- ◆ In this lab, you will use the FPGA development board “Arty” to implement a simple I/O control circuit.
  - There are 4 push-buttons and 4 yellow LED lights on the board.
  - You must design a synchronous circuit that reads each of the push-button inputs and display different light patterns.
  
- ◆ The lab file submission deadline is on 10/07 by 6:00pm.






# Buttons and LEDs on the Arty Board

Lab 4

◆ The Arty FPGA development board:

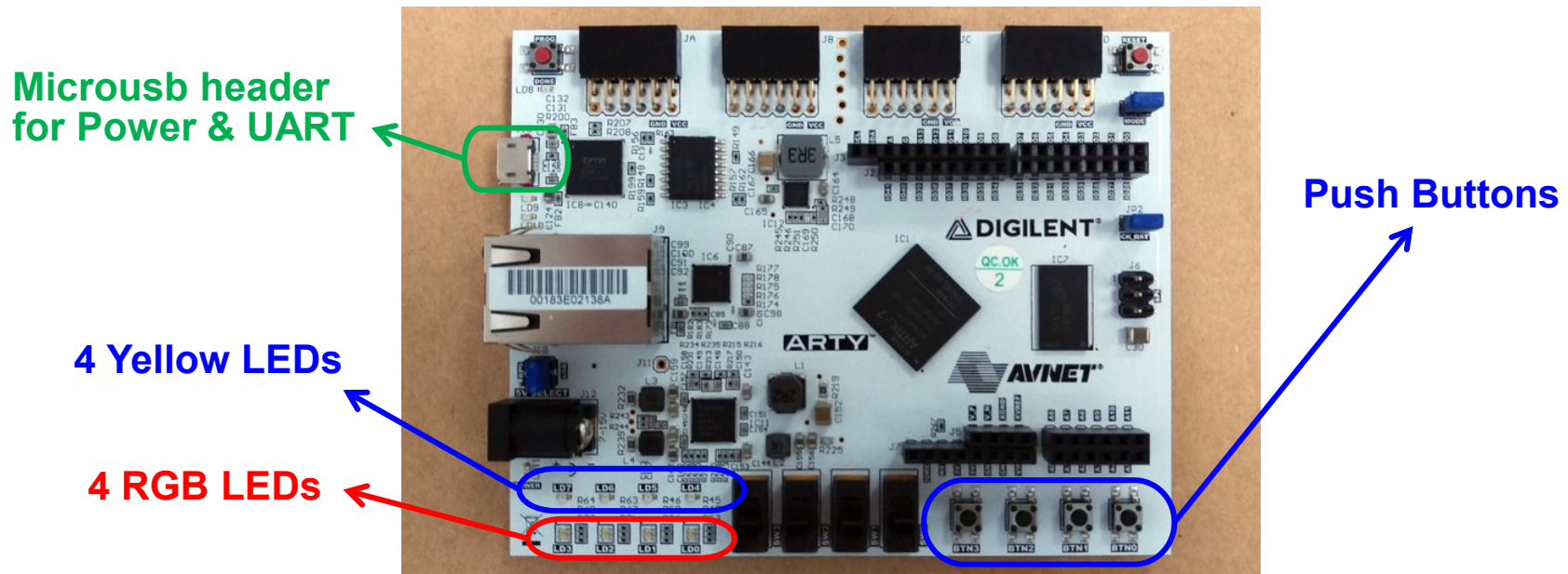

◆ We have designed an I/O daughter board for Arty.





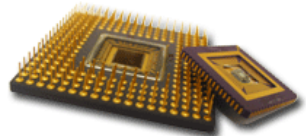
# System Behavior of Lab 4

Lab 4

- ◆ Your circuit should have a 4-bit Gray code counter register.
  - The counter value is set to  $0(0000_{\text{(gray code)}})$  upon reset.
  - The counter value is a **gray code format**.
  - The 4 LEDs display the 4 Gray code counter bits at all time.
- ◆ Push-buttons #0 and #1 are used to decrease /increase the 4-bit Gray code counter value:
  - Push the BTN0/BTN1 decrease/increase the gray code counter by 1
  - If the counter value becomes greater than  $15(1000_{\text{(gray code)}})$ , it is **truncated** to 15; if the value is smaller than  $0(0000_{\text{(gray code)}})$ , it is set to 0.
  - LD7 on FPGA board is MSB and LD4 is LSB.





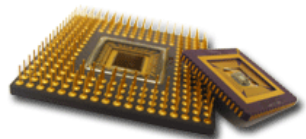
# System Behavior of Lab 4

Lab 4

- ◆ When the circuit is **first activated or reset**, set the gray code counter value to 0(0000 (gray code) ), and adjust to the lowest brightness.
- ◆ Push-buttons #2 and #3 are used to control the brightness of the LEDs.
  - BTN3 makes the LED darker and BTN2 makes it brighter by controlling PWM signal.






# User I/O Pins of an FPGA IC

Lab 4


- ◆ There are many “FPGA” pins that are used as user I/O pins: each pin connects to an I/O device such as the push-buttons or the LEDs:



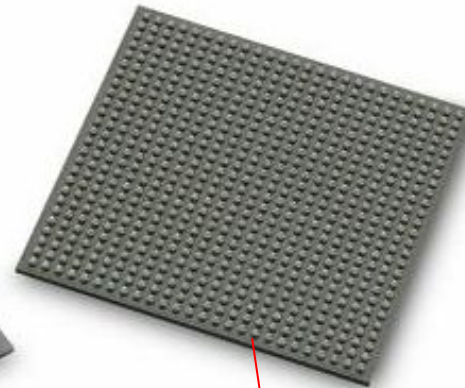Top-view of an FPGA IC  
(shows IC markings)



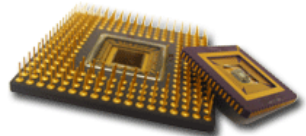Bottom-view of an FPGA IC  
(shows IC pins)






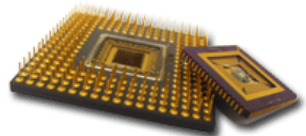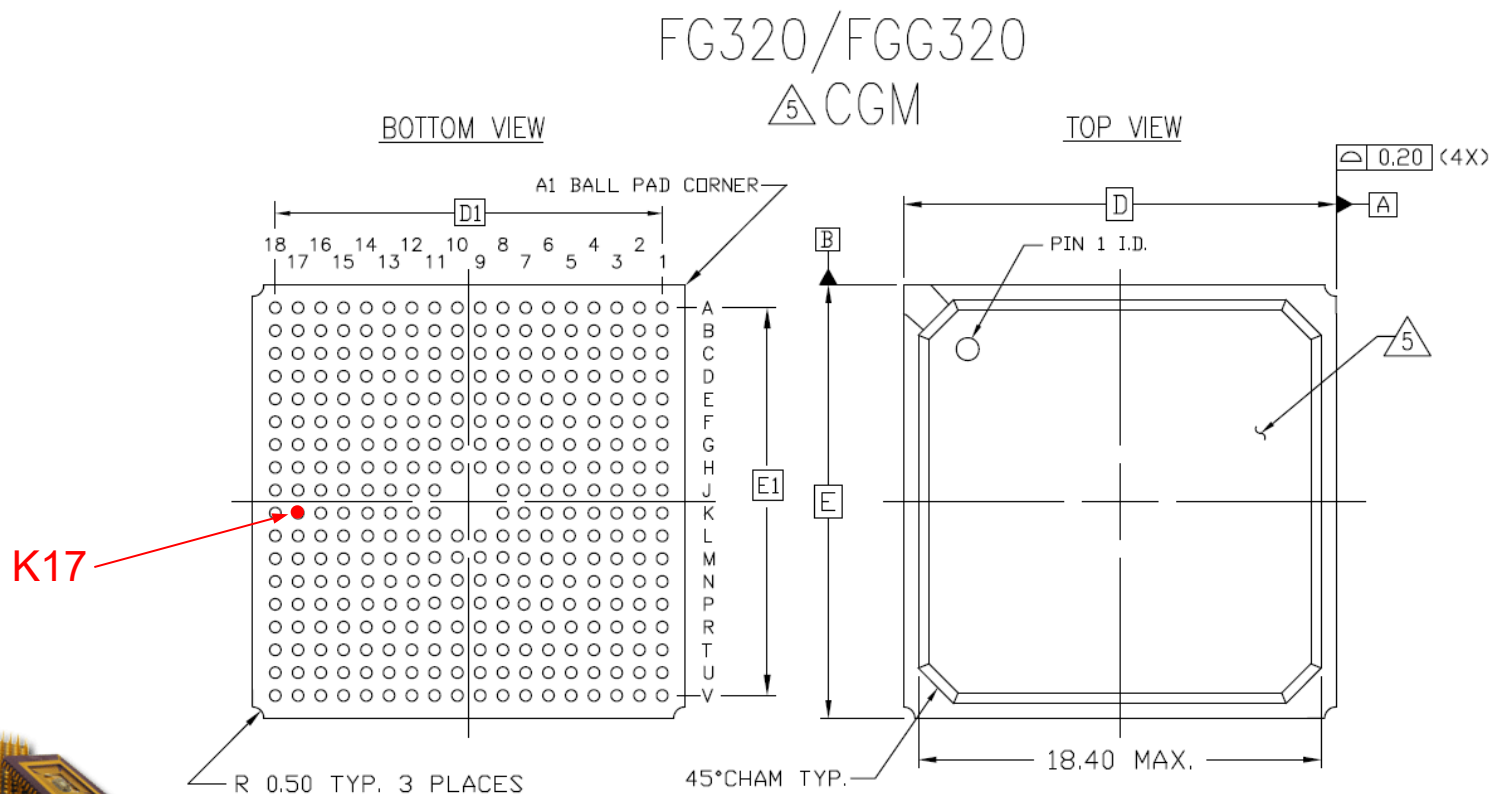
# FPGA Pin Coordinates

Lab 4

- Each pin at the bottom of the FPGA has a coordinate. For example, “K17” is the coordinate of the red pin of the Xilinx FPGA IC in the “FG320” package:







# Use the I/O Pin Signal in Verilog

Lab 4


- ◆ To read/write the I/O pins, we must map the pin coordinates to Verilog signals in our code.
  - A user constraint file, \*.xdc, is used to do the job.
- ◆ A user constraint is a text command that specifies the physical property in an HDL code. For example, for the four push-buttons, their mapping to Verilog signals can be as follows:

```
set_property -dict { PACKAGE_PIN D9 IOSTANDARD LVCMOS33 } [get_ports { usr_btn[0] }];
set_property -dict { PACKAGE_PIN C9 IOSTANDARD LVCMOS33 } [get_ports { usr_btn[1] }];
set_property -dict { PACKAGE_PIN B9 IOSTANDARD LVCMOS33 } [get_ports { usr_btn[2] }];
set_property -dict { PACKAGE_PIN B8 IOSTANDARD LVCMOS33 } [get_ports { usr_btn[3] }];
```

IC pin coordinates

Signal type

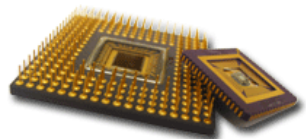Signal names to be used  
in your Verilog code!








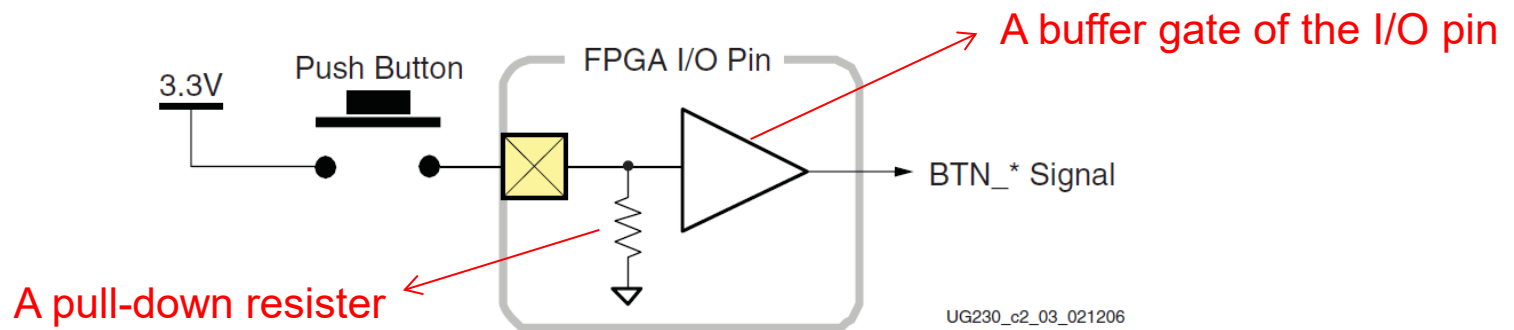
# How to Read the Input Push-Button

Lab 4

- ◆ The physical connection from an FPGA I/O pin to a push-button is as follows:



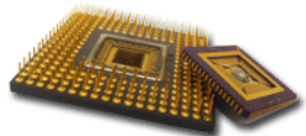- ◆ Ideally, when a push-button is pushed (the circuit is closed), the FPGA pin that connects to the button becomes high voltage and the corresponding signal in Verilog reads “1”, otherwise it reads “0”.






# Bouncing Problem



Lab 4

- ◆ In reality, however, the signal value oscillates between 0 and 1 several times before it stabilizes. This is called the bouncing behavior of a hardware button.

## The physical voltage values

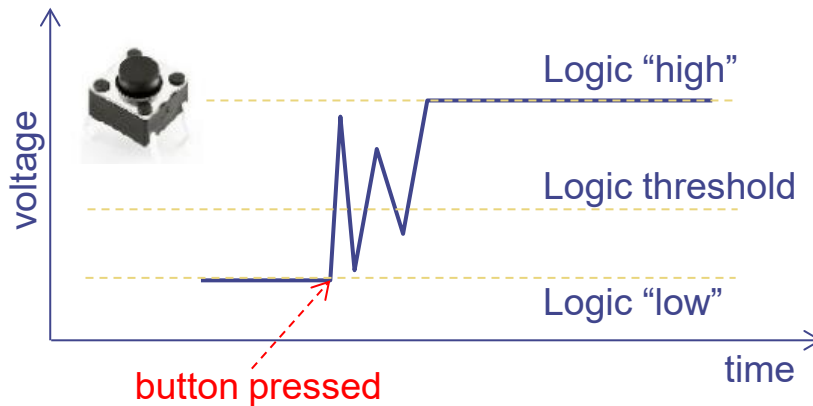

## The actual digital signal

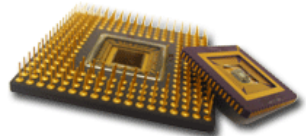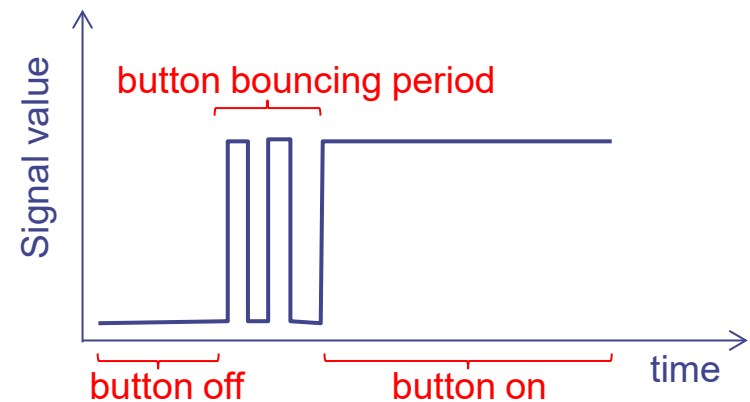



# De-bouncing Circuit


Lab 4

- ◆ To detect whether the button has been pressed, you cannot simply check the button signals:

```
always @(posedge clk, posedge reset)
  if (reset == 1)
    BTN0_is_pressed = 0;
  else
    BTN0_is_pressed = (usr_btn[0]) ? 1 : 0;
```



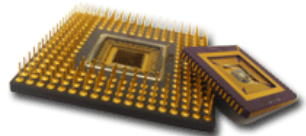- This circuit will catch all the state changes during the bouncing period → a single button click will be treated as multiple clicks!
- ◆ You must find a way to average-out the noises of the push-button signal during the bouncing period.
  - Hint: you can use a shift register to accumulate the input signal; or a timer to wait out the bouncing period.







# Turn On/Off the LEDs

Lab 4

- ◆ The LEDs can be turned on/off by writing 1/0 to the corresponding Verilog signals, `reg [3:0] usr_led`
  - The LED constraint definitions:
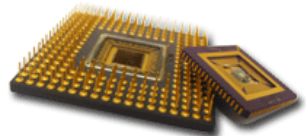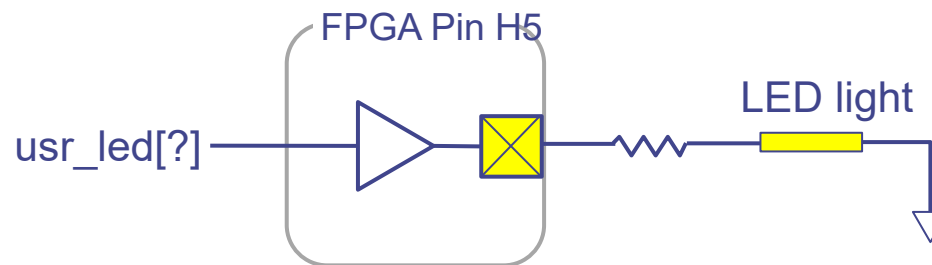
```
set_property -dict { PACKAGE_PIN H5  IOSTANDARD LVCMOS33 } [get_ports { usr_led[0] }];  
set_property -dict { PACKAGE_PIN J5  IOSTANDARD LVCMOS33 } [get_ports { usr_led[1] }];  
set_property -dict { PACKAGE_PIN T9  IOSTANDARD LVCMOS33 } [get_ports { usr_led[2] }];  
set_property -dict { PACKAGE_PIN T10 IOSTANDARD LVCMOS33 } [get_ports { usr_led[3] }];
```





# Clock and Reset Pins


Lab 4

- ◆ For synchronous design, you need a clock signal for your circuit.
  - The clock signal usually comes from an on-board oscillator.
  - There is an FPGA pin that connects to the oscillator.

```
set_property -dict {PACKAGE_PIN E3 IOSTANDARD LVCMOS33} [get_ports { clk }];
```

- ◆ For the Arty board, the reset pin is the red push button defined as follows:
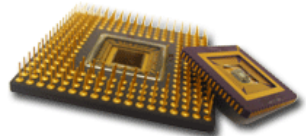
```
set_property -dict {PACKAGE_PIN C2 IOSTANDARD LVCMOS33} [get_ports { reset_n }];
```





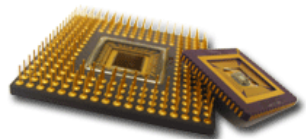
# Control of the LED Brightness

Lab 4

- ◆ The LED devices on the Arty board can only be fully lit (full power) or turned off (zero power), you can not set them to show different levels of brightness.
- ◆ To trick your eyes to see different levels of brightness, you can send a PWM signal to its power input.
- ◆ A PWM input to the LED turns it on-an-off quickly.
  - The persistence of human visions will not see flickering but only different levels of brightness, as long as your PWM frequency is high enough.






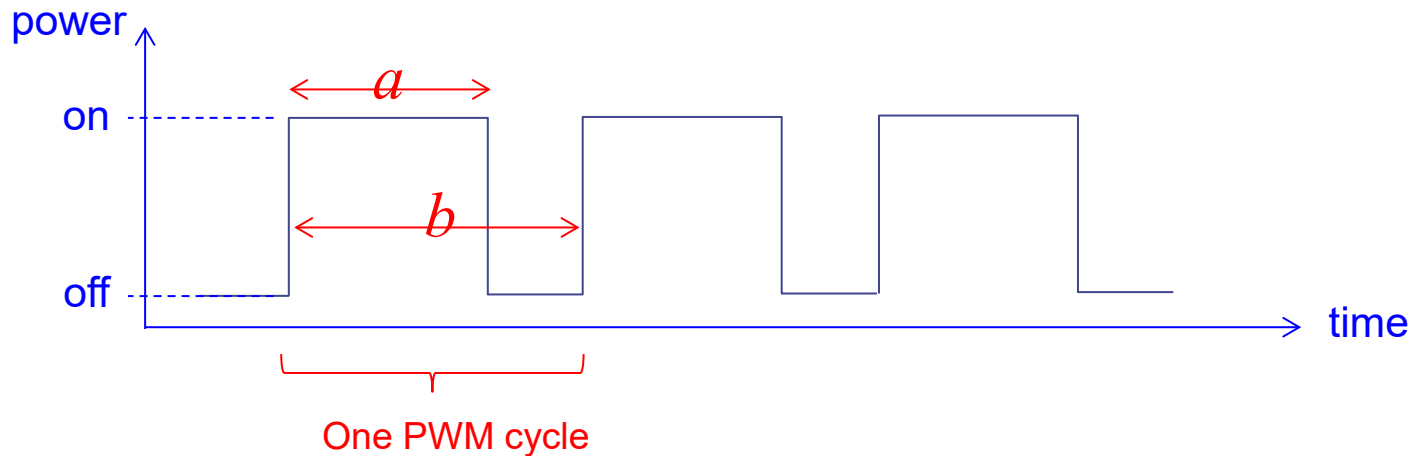
# A PWM Signal

Lab 4

- ◆ A PWM signal is simply a square wave signal:



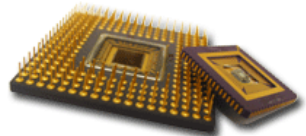- ◆ Duty-cycle: the percentage of one cycle of PWM that is in “on” state (i.e.,  $(a/b) \times 100\%$  in the figure)
  - 50% duty-cycle means the signal is “on” half of the time.







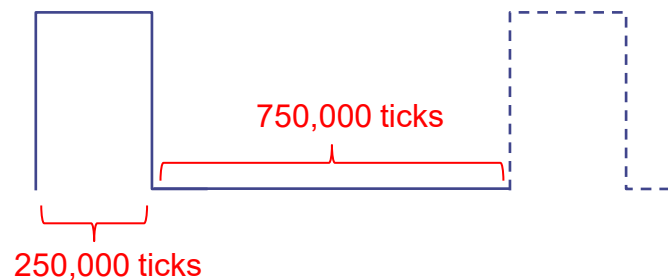
# Generation of a PWM Signal

Lab 4

- ◆ The system clock of our board is 100MHz.
  - Each second has 100,000,000 clock ticks.
- ◆ To generate a 100 Hz PWM signal, the full cycle period would be equal to 1,000,000 clock ticks.
  - The clock ticks for a 25% duty cycle PWM signal @ 100Hz would be 250,000 clock ticks for “on” period and 750,000 clock ticks for “off” period.





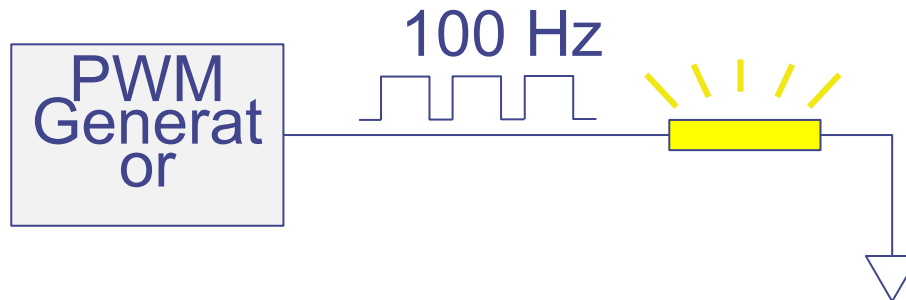
# PWM Control of Brightness

Lab 4

- ◆ Persistence of visions make most people do not see flickering when the LED is switching faster than 60 Hz.
- ◆ We can use a PWM signal higher than 60Hz to control the brightness of an LED.
- ◆ The PWM duty cycle determines the brightness.





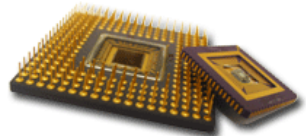
# Brightness Control for Lab 4

Lab 4

- ◆ In Lab 4, you must design a PWM signal generator circuit.
  - The PWM signal must have a frequency of 100 Hz and five different duty cycles: 5%, 25%, 50%, 75%, and 100%.
  - If LED #n should be on, the PWM signal will be assign to `usr_led[n]`.
  - If LED #n should be off, 0 will be assigned to `usr_led[n]`.
  - BTN3 decreases the current duty cycle, and BTN2 increase the current duty cycle.






# Sample Project of Lab 4

Lab 4

- ◆ A sample project, lab4.zip, is available on E3.
  - The constraint file for Arty is provided to you in this project.
- ◆ The project has a circuit that lights up LED 0 ~ 3 when you press BTN 0 ~ 3, respectively.

```
module lab4(  
    input  clk,           // System clock at 100 MHz  
    input  reset_n,       // System negative reset signal  
    input  [3:0] usr_btn,  // Four user pushbuttons  
    output [3:0] usr_led   // Four yellow LEDs  
);  
  
assign usr_led = usr_btn;  
endmodule
```

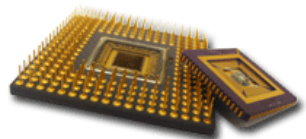- ◆ There is no de-bouncing circuit for the button inputs so you have to add this part by yourself.





# Generating the Programming File

Lab 4

- ◆ To test the design on Arty, you must generate the programming file “lab4.bit” for the FPGA:

The screenshot shows the Vivado 2017.2.1 IDE interface. The top menu bar includes File, Edit, Flow, Tools, Window, Layout, View, and Help. The top right corner displays 'write\_bitstream Complete' with a green checkmark. The left sidebar contains the 'PROJECT MANAGER' section with options like Settings, Add Sources, Language Templates, IP Catalog, IP INTEGRATOR, SIMULATION, RTL ANALYSIS, SYNTHESIS, IMPLEMENTATION, and PROGRAM AND DEBUG. The 'PROGRAM AND DEBUG' section is highlighted with a red dashed circle, and the 'Generate Bitstream' option is selected. The main workspace is divided into three panes: 'Sources' (showing 'Design Sources (1)' and 'Constraints (1)' with 'arty\_base.xdc' selected), 'Source File Property' (showing 'arty\_base.xdc' with 'General' and 'Properties' tabs), and 'lab4.v' (showing the Verilog code for 'module lab3'). The 'lab4.v' code is as follows:

```
22
23 module lab3(
24     input  clk,           // System clock at 100 MHz
25     input  reset_n,       // System reset signal, in negative logic
26     input  [3:0] usr_btn, // Four user pushbuttons
27     output [3:0] usr_led  // Four yellow LEDs
28 );
29
30 assign usr_led = usr_btn;
31
32 endmodule
33
```

A red dashed arrow points from the 'Generate Bitstream' option in the 'PROGRAM AND DEBUG' section to the 'lab4.v' file in the 'Sources' pane. The bottom status bar shows the 'Design Runs' table:

Name	Constraints	Status	WNS	TNS	WHS	THS	TPWS	Total Power	Failed Routes	LUT	FF
✓ synth_1	constrs_1	synth_design Complete!								0	0
✓ impl_1	constrs_1	write_bitstream Complete!	NA	NA	NA	NA	NA	0.065	0	0	0



# Downloading Your Circuit to the Board

Lab 4

- ◆ To download your programming file into the FPGA, you must use the “Hardware Manager” :

The screenshot shows the Vivado 2017.2.1 IDE. The 'Hardware Manager' window is open, displaying 'No hardware target is open. Open target'. The 'Open Target' button is highlighted with a red dashed circle and an arrow. The 'Tcl Console' window shows the following instructions:

```
1. Make sure the clock connected to the debug hub (dbg_hub) core is a free running clock and is not gated.
2. Make sure the BSCAN_SWITCH_USER_MASK device property in Vivado Hardware Manager reflects the current target.
For more details on setting the scan chain property, consult the Vivado Debug and Programming User Guide.
```

Below the instructions, the Tcl commands `close_hw` and `open_hw` are listed. The 'Program Device' button is also visible.

At the bottom left, there is a small image of an FPGA board. Below it, the text reads: 打开硬件程序和调试管理

At the bottom right, a red text overlay says: Plug the Arty USB cable into a PC, click “Open Target” then “Auto Connect”





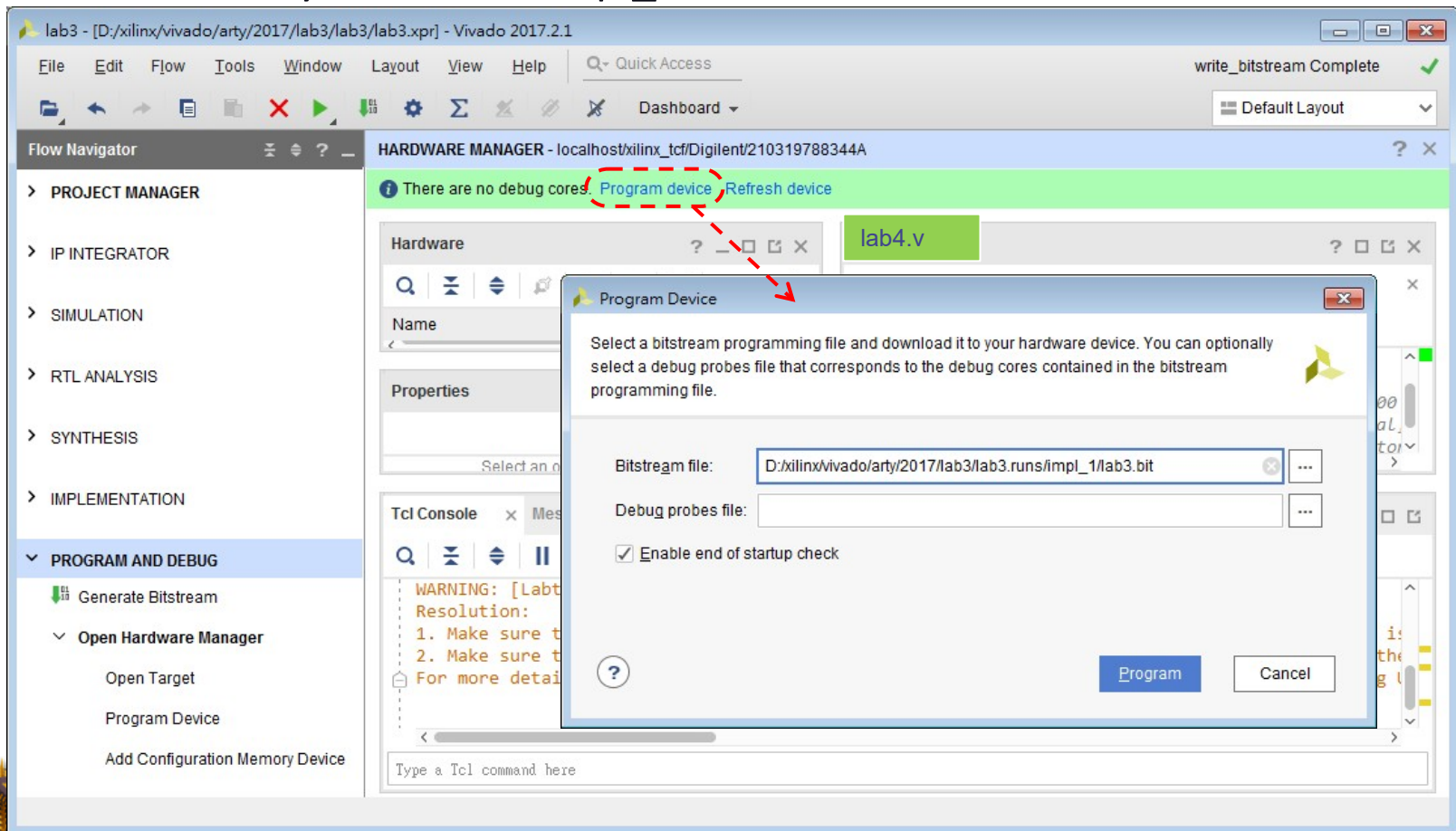
# Program the FPGA

Lab 4

- ◆ Hit “Program device” then browse to the \*.bit file:
  - The bit file is under <project directory>/lab4.run/impl\_1/lab4.bit








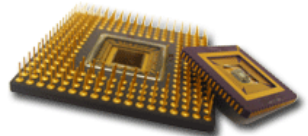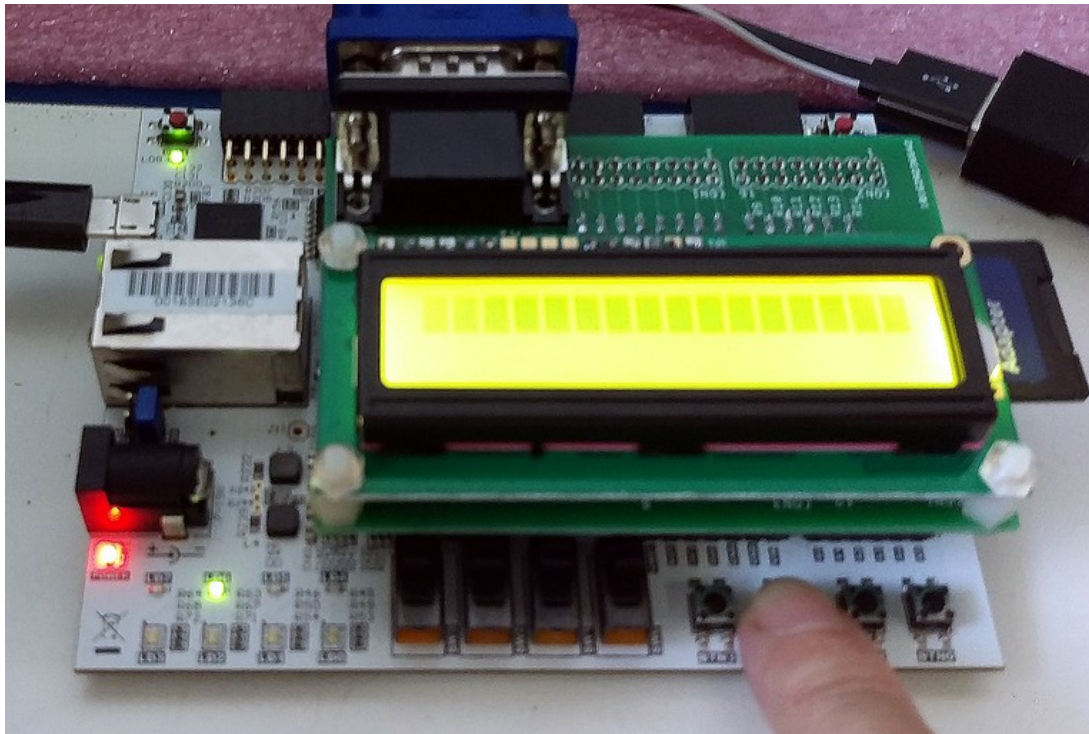
# Test Your Design

Lab 4

- ◆ You can now test your circuit by clicking the buttons on the Arty board and see how the LEDs lights up!





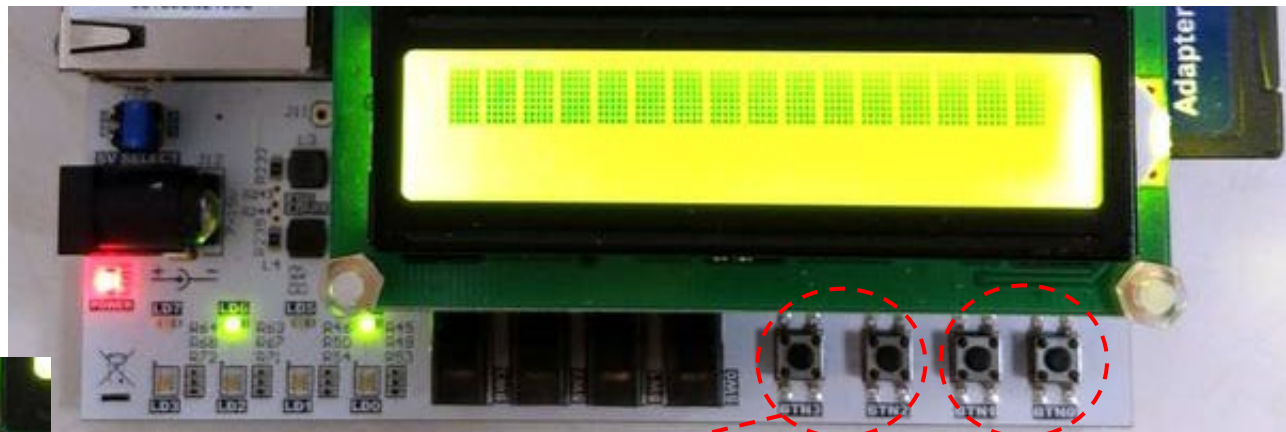
# What You Need to Do for Lab 4

Lab 4

- ◆ Design a circuit to display the value of a 4-bit Gray code counter on the LEDs with different brightness.
  - BTN1/BTN0 increases/decreases the counter value.
  - BTN2/BTN3 increases/decreases the brightness of the LEDs (all four LEDs should have the same brightness).
  - De-bouncing CKT
  - PWM CKT



← Increase/decrease the brightness of LEDs with five different brightness levels

→ Increase/decrease the 4-bit Gray code counter value